

Corrigé du DM1

1FTP

Exercise 1

$$\begin{aligned} 1) & (100 + 5) \times 2 \\ & = 100 \times 2 + 5 \times 2 \\ & = 200 + 10 \\ & = 210 \end{aligned}$$


$$\begin{aligned} 2) & 100 + 5 \times 2 \\ & = 100 + 10 \\ & = 110 \end{aligned}$$

$$\begin{aligned} 3) & 13 + 7 \times 2 - 5 \\ & = 13 + 14 - 5 \\ & = 22 \end{aligned}$$

$$\begin{aligned} 4) & (13 + 7) (2 - 5) \\ & = 20 (-3) \\ & = -60 \end{aligned}$$

$$\begin{aligned} 5) & 8 \times 4 + 3 \times 2 \\ & = 32 + 6 \\ & = 38 \end{aligned}$$

$$\begin{aligned} 6) & 8 \times (4 + 3) \times 2 \\ & = 8 \times 7 \times 2 \\ & = 112 \end{aligned}$$
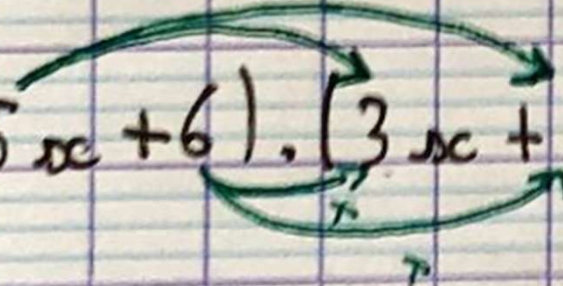
$$7) = (5x + 6) \cdot (3x + 2)$$


$$= 5x \cdot 3x + 5x \cdot 2 + 6 \cdot 3x + 6 \cdot 2$$

$$= 15x^2 + 10x + 18x + 12$$

$$= 15x^2 + 28x + 12$$

$$\begin{aligned} 8) &= 5x + 6 \cdot (3x + 2) \\ &= 5x + 6 \cdot 3x + 6 \cdot 2 \\ &= 5x + 18x + 12 \\ &= 23x + 12 \end{aligned}$$

$$\begin{aligned} 9) &= 2 - 1(2R + 5) \\ &= 2 - 2R - 5 \\ &= -2R - 3 \end{aligned}$$

$$\begin{aligned} 10) &= 3y + x \cdot (y^2 - 2y) \\ &= 3y + y^2 x + (-2yx)x \\ &= 3y + y^2 x - 2yx \end{aligned}$$

$$\begin{aligned} 11) &= 3y + x y^2 - 2y \\ &= 3y - 2y + x y^2 \\ &= y + x y^2 \end{aligned}$$

Exercice 2

$$\text{Donc } \frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\text{On voit que } \frac{a}{b} + \frac{c}{d} = \frac{ad + cb}{bd}$$

$$\frac{1}{R_e} = \frac{1R_2 + 1R_1}{R_2 \times R_2} = \frac{R_2 + R_1}{R_2 \times R_2} \quad \text{donc } R_e \text{ vaut l'inverse, ça donne}$$

$$R_e = \frac{R_2 \times R_1}{R_2 + R_1}$$

Exercise 3

$$1) \quad V_{R2} = V_{CC} \cdot \frac{R_2}{R_2 + R_1}$$

$$V_{CC} = \frac{V_{R2}}{\frac{R_2}{R_2 + R_1}}$$

$$V_{CC} = \frac{V_{R2} (R_2 + R_1)}{R_2}$$

2)

$$V_{R2} = V_{CC} \cdot \frac{R_2}{R_2 + R_1}$$

$$V_{R2} (R_2 + R_1) = V_{CC} \cdot R_2$$

$$V_{R2} \cdot R_2 + V_{R2} \cdot R_1 = V_{CC} \cdot R_2$$

$$V_{R2} \cdot R_1 = V_{CC} \cdot R_2 - V_{R2} \cdot R_2$$

$$V_{R2} \cdot R1 = R2 (V_{CC} - V_{R2})$$

$$R2 = \frac{V_{R2} \cdot R1}{V_{CC} - V_{R2}}$$

On calcule $R2$:

$$R2 = \frac{2 \times 4 \times 10^3}{5 - 2}$$

$$= \frac{2 \times 10^3}{3}$$

$$\approx 666,7 \Omega \approx 7 \times 10^2 \text{ k}\Omega$$

Pour obtenir $V_{R2} = 2V$, il faut que $R2 = 7 \times 10^2 \Omega$

2)

$$V_{R_2} = V_{CC} \times \frac{R_2}{R_2 + R_1}$$

$$\Rightarrow V_{R_2} \times (R_2 + R_1) = V_{CC} \times R_2$$

$$\Rightarrow V_{R_2} \times R_2 + V_{R_2} \times R_1 = V_{CC} \times R_2$$

$$\Rightarrow V_{R_2} \times R_2 - V_{CC} \times R_2 = -V_{R_2} \times R_1$$

$$\Rightarrow R_2 \times (V_{R_2} - V_{CC}) = -V_{R_2} \times R_1$$

$$\Rightarrow R_2 = \frac{(-V_{R_2} \times R_1)}{V_{R_2} - V_{CC}}$$

maintenant maintenant que $V_{R_2} = 2V$ que $V_{cc} = 5V$ et que $R_1 = 1000 \Omega$

$$\text{soit } R_2 = \frac{(-2V \times 1000 \Omega)}{2V - 5V}$$

$$R_2 = \frac{-2000 \Omega}{-3V}$$

$$R_2 = \frac{2000 \Omega}{3V}$$

$$R_2 = 666,67 \Omega$$